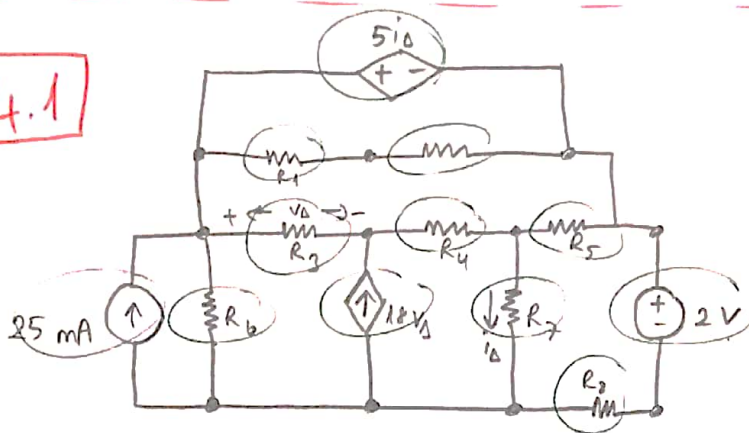


4.1




- a) Branches \rightarrow 12 branches
- b) Branches where the current is unknown \rightarrow Every branch except 25 mA branch.
- c) Essential branches \rightarrow 10 essential branches.

- d) Essential branches where the current is unknown \rightarrow 9 essential branches.
- e) Nodes \rightarrow 7 nodes
- f) Essential nodes \rightarrow 5 essential nodes
- g) Meshes \rightarrow 6 meshes

4.2

- a) Essential branches where the current is unknown \rightarrow There are 9 so we need 9 equations.
- b) We can apply KCL \rightarrow 4 essential nodes.
- c) 4 equations must be derived using KVL.
- d) We should avoid where the current source occurs. At the bottom, there are two meshes containing a current source. We cannot determine the voltage across that current source.

4.3

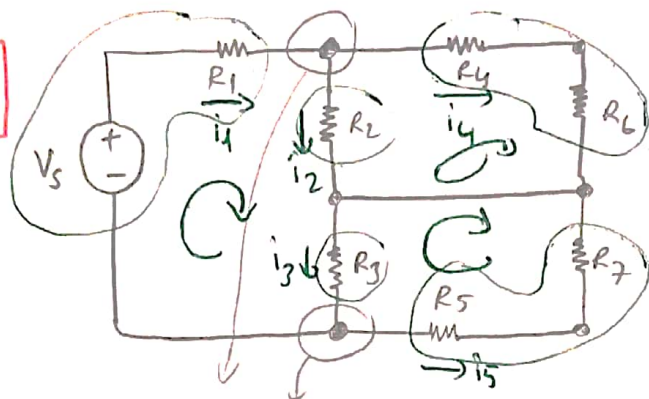

a) There are 8 circuit components. But R_4-R_6 , R_5-R_7 , and V_s-R_1 are series. So we have $8-3=5$ unknown currents.

b) There are two independent KCL equations.

c) $i_1 = i_2 + i_4$, $i_3 = i_1 + i_5$

d) There are 3 meshes. So we can write three independent KVL equations.


e) $-V_s + R_1 i_1 + R_2 i_2 + R_3 i_3 = 0$

$$R_4 i_4 + R_6 i_6 - R_2 i_2 = 0$$

$$R_3 i_3 + R_5 i_5 + R_7 i_7 = 0$$

4.4

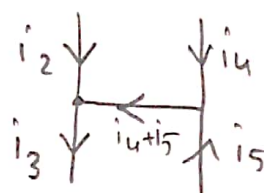a) 1. $i_2 + i_4 - i_1 = 0$
 2. $i_1 + i_5 - i_3 = 0$
 3. $i_2 + i_4 + i_5 - i_3 = 0$




b) If we add 1. and 2. equations

$$(i_2 + i_4 - i_1) + (i_1 + i_5 - i_3) = i_2 + i_4 + i_5 - i_3$$

We can reach 3. equation.

4.11

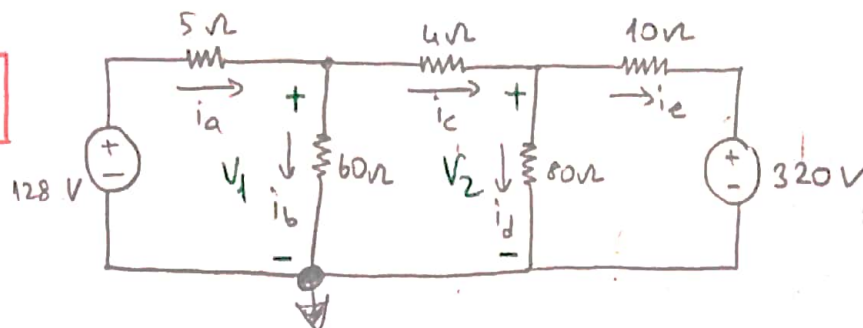

$$a) \frac{V_1 - 128}{5} + \frac{V_1}{60} + \frac{V_1 - V_2}{4} = 0 \rightarrow \frac{12V_1 - 128 \cdot 12 + V_1 + 15V_1 - 15V_2}{60} = 0$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{80} + \frac{V_2 - 320}{10} = 0 \rightarrow \frac{20V_2 - 20V_1 + V_2 + 8V_2 - 320 \cdot 8}{80} = 0$$

$$\text{Result} \rightarrow V_1 = 162 \text{ V}$$

$$V_2 = 200 \text{ V}$$

$$i_a = \frac{128 - V_1}{5} = \underline{\underline{-6.8 \text{ A}}}$$

$$i_c = \frac{V_1 - V_2}{4} = \underline{\underline{-9.5 \text{ A}}}$$

$$i_b = \frac{V_1}{60} = \underline{\underline{2.7 \text{ A}}}$$


$$i_d = \frac{V_2}{80} = \underline{\underline{2.5 \text{ A}}}$$

$$i_e = \frac{V_2 - 320}{10} = \underline{\underline{-12 \text{ A}}}$$

$$b) \boxed{P = V \cdot I = \frac{V^2}{R} = I^2 \cdot R}$$

$$P_{320V} = 320 \cdot i_e = 320 \cdot (-12) = \underline{\underline{-3840 \text{ W}}}$$

4.12

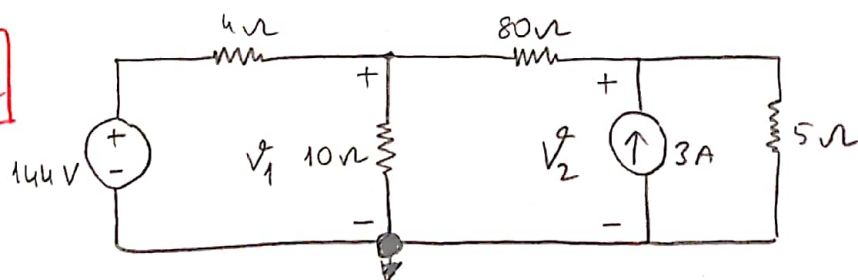

$$V_1^? = ?$$

$$V_2^? = ?$$


$$\frac{V_1^? - 144}{4} + \frac{V_1^?}{10} + \frac{V_1^? - V_2^?}{80} = 0 \rightarrow \frac{20V_1^? - 144 \cdot 20 + 8V_1^? + V_1^? - V_2^?}{80} = 0$$

$$-3 + \frac{V_2^? - V_1^?}{80} + \frac{V_2^?}{5} = 0 \rightarrow \frac{80 \cdot (-3) + V_2^? - V_1^? + 16V_2^?}{80} = 0$$

$$\text{Result} \rightarrow V_1^? = 100 \text{ V}$$

$$V_2^? = 20 \text{ V} //$$

4.15

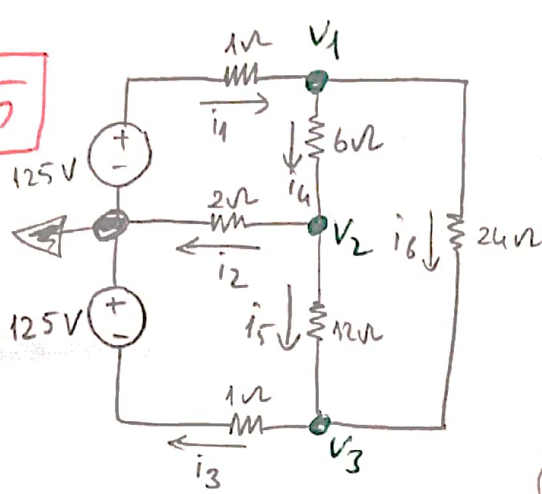

$$i_1 = \frac{125 - V_1}{1} = \underline{\underline{23.76 \text{ A}}}$$

$$i_2 = \frac{V_2}{2} = \underline{\underline{5.33 \text{ A}}}$$

$$i_3 = \frac{V_3 + 125}{1} = \underline{\underline{18.43 \text{ A}}}$$

$$i_4 = \frac{V_1 - V_2}{6} = \underline{\underline{15.10 \text{ A}}}$$

$$i_5 = \frac{V_2 - V_3}{12} = \underline{\underline{9.77 \text{ A}}}$$

$$a) \frac{V_1 - 125}{1} + \frac{V_1 - V_2}{6} + \frac{V_1 - V_3}{24} = 0$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{2} + \frac{V_2 - V_3}{12} = 0$$

$$\frac{V_3 + 125}{1} + \frac{V_3 - V_2}{12} + \frac{V_3 - V_1}{24} = 0$$

$$24V_1 - 125 \cdot 24 + 4V_1 - 4V_2 + V_1 - V_3 = 0$$

$$2V_2 - 2V_1 + 6V_2 + V_2 - V_3 = 0$$

$$24V_3 + 125 \cdot 24 + 2 \cdot V_3 - 2V_2 + V_3 - V_1 = 0$$

$$V_1 = \underline{\underline{101.24 \text{ V}}} \quad V_2 = \underline{\underline{10.66 \text{ V}}} \quad V_3 = \underline{\underline{-106.57 \text{ V}}}$$


$$i_6 = \frac{V_1 - V_3}{24} = \underline{\underline{8.66 \text{ A}}}$$

$$b) P_{\text{developed}} = 125 i_1 + 125 i_3 = 125 \cdot (23.76) + 125 \cdot (18.43) = 5273.09 \text{ W}$$

$$P_{\text{dissipated}} = i_1^2 \cdot 1 + i_4^2 \cdot 6 + i_2^2 \cdot 2 + i_5^2 \cdot 12 + i_3^2 \cdot 1 + i_6^2 \cdot 24 = 5273.09 \text{ W}$$

same

4.24

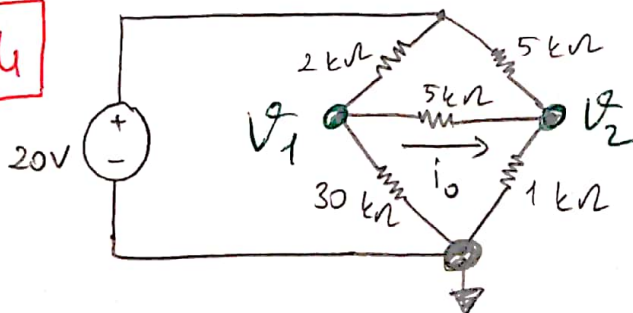

$$V_1 + 6V_1 - 6V_2 + 15V_1 - 20 \cdot 15 = 0$$

$$5V_2 + V_2 - V_1 + V_2 - 20 = 0$$

$$V_1 = 15 \text{ V} \quad V_2 = 5 \text{ V}$$


$$i_0 = \frac{V_1 - V_2}{5 \text{ k}} = \frac{15 - 5}{5000}$$

$$= \underline{\underline{0.002 \text{ A}}}$$

$$\frac{V_1}{30 \text{ k}} + \frac{V_1 - V_2}{5 \text{ k}} + \frac{V_1 - 20}{2 \text{ k}} = 0$$

$$\frac{V_2}{1 \text{ k}} + \frac{V_2 - V_1}{5 \text{ k}} + \frac{V_2 - 20}{5 \text{ k}} = 0$$

4.27

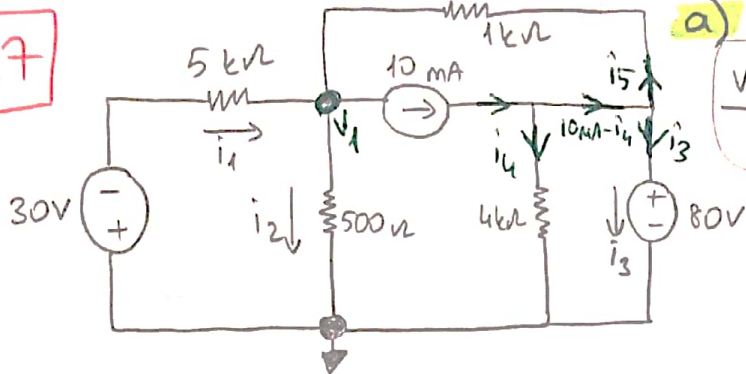

a)

$$\frac{V_1 + 30}{5k} + \frac{V_1}{500} + \frac{V_1 - 80}{1k} + \frac{0.01}{1} = 0$$

$$V_1 + 30 + 10V_1 + 5V_1 - 80.5 + 50 = 0$$

$$V_1 = 20 \text{ V}$$

$$i_4 = \frac{80}{4k} = 20 \text{ mA}$$

$$i_5 = \frac{80 - V_1}{1k} = 60 \text{ mA}$$

$$i_1 = \frac{-30 - V_1}{5k} = -10 \text{ mA} = -0.01 \text{ A}$$

$$i_2 = \frac{V_1}{500} = 40 \text{ mA} = 0.04 \text{ A}$$

$$10 \text{ mA} - i_4 = i_5 + i_3$$

$$10 \text{ mA} - i_4 - i_5 = i_3$$

$$10 \text{ mA} - 20 \text{ mA} - 60 \text{ mA} = i_3 = -70 \text{ mA} = -0.07 \text{ A}$$

b) $P_{30V} = V \cdot I = 30 \cdot (-0.01) = -0.3 \text{ W}$

$$P_{5k} = I^2 \cdot R = (0.01)^2 \cdot 5k = 0.5 \text{ W}$$

$$P_{500\Omega} = I^2 \cdot R = (0.04)^2 \cdot 500 = 0.8 \text{ W}$$

$$P_{10mA} = V \cdot I = (V_1 - 80) \cdot (0.01) = -0.6 \text{ W}$$

$$P_{4k} = I^2 \cdot R = (0.02)^2 \cdot (4000) = 1.6 \text{ W}$$

$$P_{80V} = V \cdot I = 80 \cdot (-0.07) = -5.6 \text{ W}$$

$$P_{1k} = I^2 \cdot R = (0.06)^2 \cdot (1000) = 3.6 \text{ W}$$


dissipated

$$-0.3 - 0.6 - 5.6 = -6.5 \text{ W}$$

$$0.5 + 0.8 + 1.6 + 3.6 = 6.5 \text{ W}$$

developed

4.30

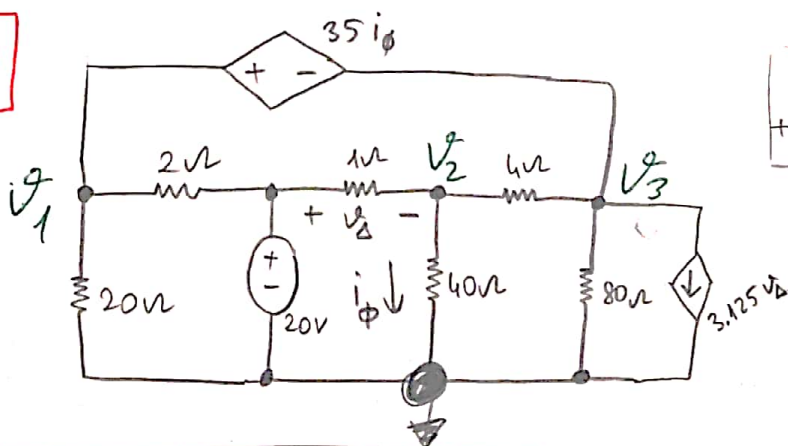

$$4V_1 + 40V_1 - 20.40 + 20V_3 + 20(-V_2) + V_3 + 3.125V_\Delta \cdot 80 = 0$$

$$V_2 + 10V_2 - 10V_3 + 40V_2 - 800 = 0$$

$$V_\Delta = \frac{20 - V_2}{1}$$

$$\frac{V_2}{40} = i_\phi$$

$$V_1 - V_3 = 35i_\phi$$

$$\frac{V_1}{20} + \frac{V_1 - 20}{2} + \frac{V_3 - V_2}{4} + \frac{V_3}{80} + 3.125V_\Delta = 0$$

$$\frac{V_2}{40} + \frac{V_2 - V_3}{4} + \frac{V_2 - 20}{1} = 0$$

$$V_1 = -20.25 \text{ V}$$


$$V_2 = 10 \text{ V}$$

$$V_3 = -29 \text{ V}$$

$$P_{\text{developed } 20V} = V \cdot I = 20 \cdot \left(\frac{20 - V_1}{2} + \frac{20 - V_2}{1} \right)$$

$$= 20 \cdot (30.125) = 602.5 \text{ W}$$

4.36

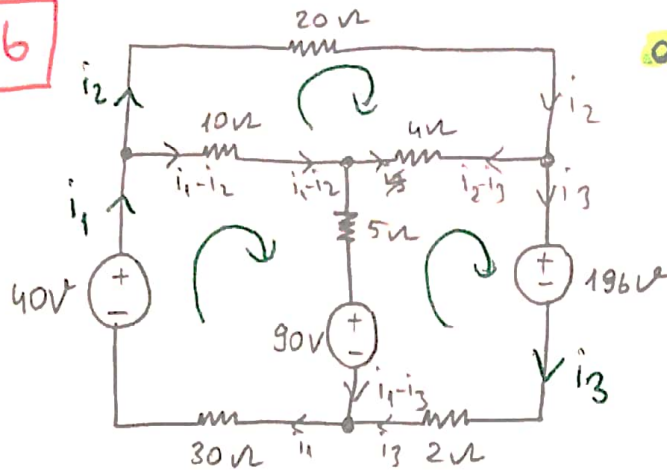

a)

$$40 + 10(i_1 - i_2) + 5(i_1 - i_3) + 90 + 30i_1 = 0$$

$$20i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$196 + 2i_3 - 90 + 5(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$i_1 = -5A \quad i_2 = -3A \\ i_3 = -13A$$

b) $P_{20\Omega} = I^2 \cdot R = (-3)^2 \cdot 20 = 180W$

$$P_{10\Omega} = I^2 R = (-5+3)^2 \cdot 10 = 40W$$

$$P_{4\Omega} = I^2 R = (-3+13)^2 \cdot 4 = 400W$$

$$P_{5\Omega} = I^2 R = (-5+13)^2 \cdot 5 = 320W$$

$$P_{30\Omega} = I^2 R = (-5)^2 \cdot 30 = 750W$$

$$P_{2\Omega} = I^2 R = (-13)^2 \cdot 2 = 338W$$


$$P_{90V} = V \cdot I = 90(-5+13) = 720W$$

$$P_{\text{dissipated}} = 2748W$$


$$P_{40V} = V \cdot I = 40 \cdot (-5) = -200W$$

$$P_{196V} = V \cdot I = 196 \cdot (-13) = -2548W$$

$$P_{\text{developed}} = -2748W$$

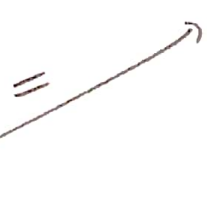

4.39

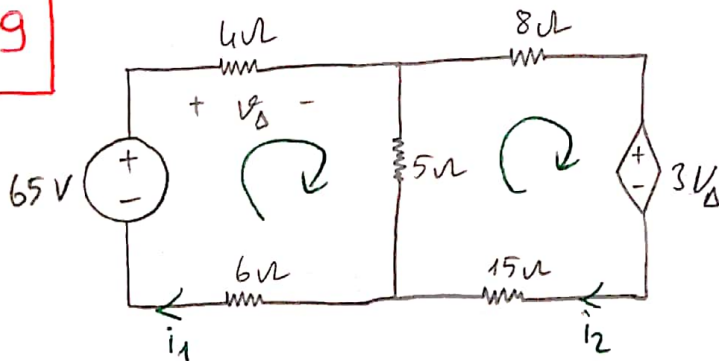

$$-65 + 4i_1 + 5(i_1 - i_2) + 6i_1 = 0$$

$$8i_2 + 3V_{\Delta} + 15i_2 + 5(i_2 - i_1) = 0$$


$$V = I \cdot R$$

$$V_{\Delta} = i_1 \cdot 4$$

$$i_1 = 4A, \quad i_2 = -1A, \quad V_{\Delta} = 16V$$

$$P_{15\Omega} = I^2 \cdot R = (-1)^2 \cdot 15 = 15W$$

4.46

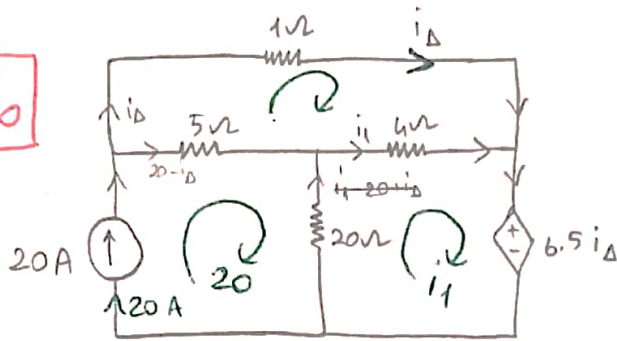

$$24i_1 + 6.5i_\Delta - 4i_\Delta - 20 \cdot 20 = 0$$


$$(5+4+1)i_\Delta - 4i_1 - 5 \cdot 20 = 0$$

$$i_1 = 15A \quad i_\Delta = 16A$$

$$P_{20A} = I \cdot V = 20 \cdot (7.5 \cdot 16)$$

$$= 2400W$$

4.47

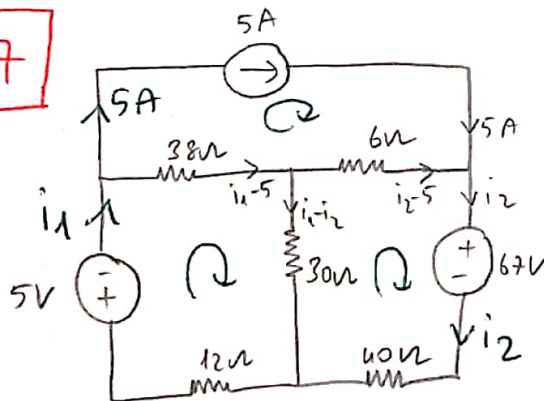

$$a) \quad 5 + 38 \cdot (i_1 - 5) + 30 \cdot (i_1 - i_2) + 12i_1 = 0$$

$$67 + 40i_2 + 30(i_2 - i_1) + 6(i_2 - 5) = 0$$

$$i_1 = 2.5A \quad i_2 = 0.5A$$

$$P_{5A} = I \cdot V = 5 \cdot (38 \cdot (i_1 - 5) + 6 \cdot (i_2 - 5))$$

$$P_{5A} = 5 \cdot (-122) = \underline{\underline{-610W}}$$

$$b) \quad P_{5V} = V \cdot I = 5 \cdot i_1 = 5 \cdot (2.5) = 12.5W$$

$$P_{67V} = V \cdot I = 67 \cdot i_2 = 67 \cdot (0.5) = 33.5W$$

They are all positive. So $P_{\text{delivered}} = P_{5A} = \underline{\underline{-610W}}$

$$c) \quad P_{38\Omega} = I^2 R = (i_1 - 5)^2 \cdot 38$$

$$P_{6\Omega} = I^2 R = (i_2 - 5)^2 \cdot 6$$


$$P_{30\Omega} = I^2 R = (i_1 - i_2)^2 \cdot 30$$

$$P_{12\Omega} = I^2 R = i_1^2 \cdot 12$$

$$P_{40\Omega} = I^2 R = i_2^2 \cdot 40$$

$$+ 46 = \underline{\underline{610W}} = P_{\text{dissipated}}$$

4.54

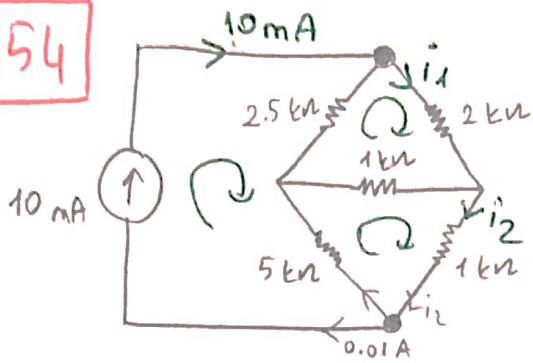

a) There are three meshes and one of the meshes has known current. So we should use mesh analysis.




$$\begin{aligned} b) \quad & 2.5k \cdot (i_1 - 0.01) + 2k(i_1) + 1k(i_1 - i_2) = 0 \\ & 5k(i_2 - 0.01) + 1k(i_2 - i_1) + 1ki_2 = 0 \end{aligned} \rightarrow \begin{aligned} i_1 &= 0.006 \text{ A} \\ i_2 &= 0.008 \text{ A} \end{aligned}$$

Hint: $P_{1k\Omega} = I^2 \cdot R = (i_1 - i_2) \cdot R = (0.006 - 0.008)^2 \cdot 1000 = \underline{\underline{-0.004 \text{ W}}}$

c) No. Because mesh analysis is easy method to find current. I choose this method again.

$$\begin{aligned} d) \quad P_{\text{delivered } 10\text{mA}} &= I \cdot V = (0.01) \cdot (2k \cdot i_1 + 1ki_2) \\ &= (0.01) \cdot (2000 \cdot (0.006) + 1000 \cdot (0.008)) \\ &= \underline{\underline{0.2 \text{ W}}} \end{aligned}$$

4.59

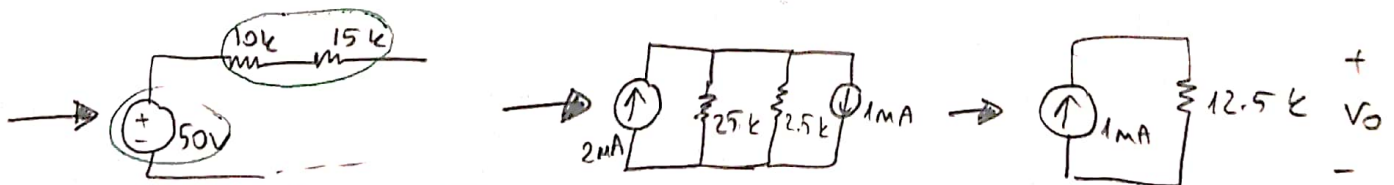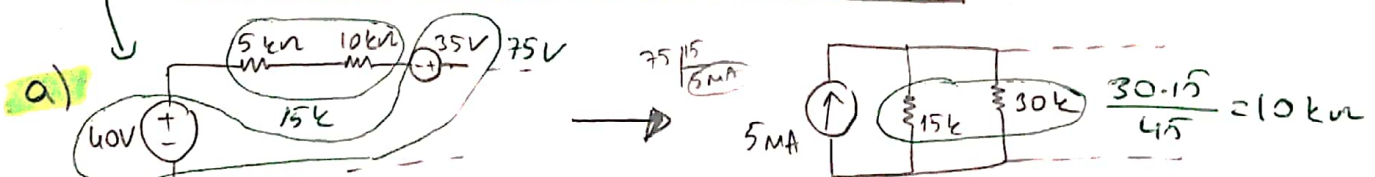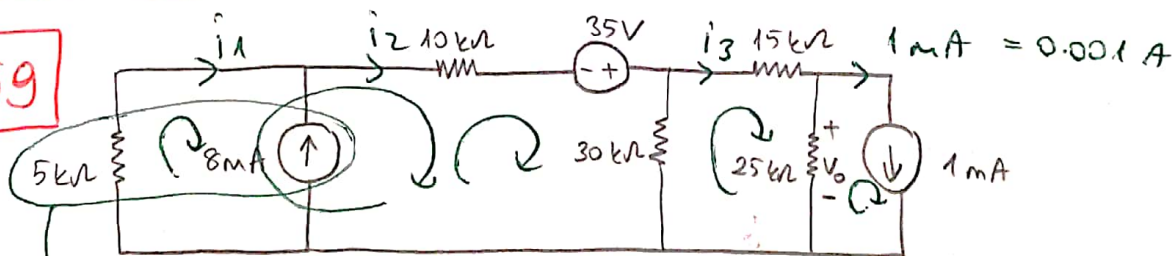


$$\begin{aligned} b) \quad & 5ki_1 + (30k + 10k)i_2 - 30ki_3 - 35 = 0 \\ & 0.008 + i_1 = i_2 \\ & 30k(i_3 - i_2) + 15ki_3 + 25k \cdot (i_3 - 0.001) = 0 \\ & i_1 = -5.33 \text{ mA} \quad i_2 = 2.67 \text{ mA} \quad i_3 = 1.5 \text{ mA} \end{aligned}$$

$$\begin{aligned} V &= I \cdot R \\ V_0 &= (0.001) \cdot (12500) \\ V_0 &= \underline{\underline{12.5 \text{ V}}} \end{aligned}$$


$$\begin{aligned} V_0 &= I \cdot R = (1.5 - 0.001) \cdot 25k \\ &= \underline{\underline{12.5 \text{ V}}} \end{aligned}$$

4.64

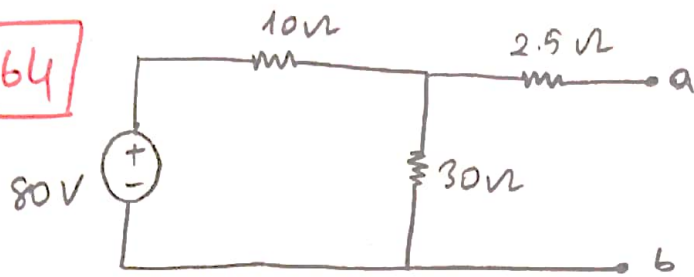


$$V_{Th} = \frac{30}{40} \cdot 80 = \underline{\underline{60V}}$$
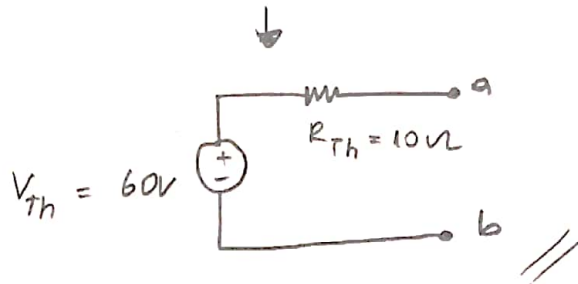
$$R_{Th} = 2.5 + \frac{10 \cdot 30}{10 + 30} = \underline{\underline{10\Omega}}$$



4.78

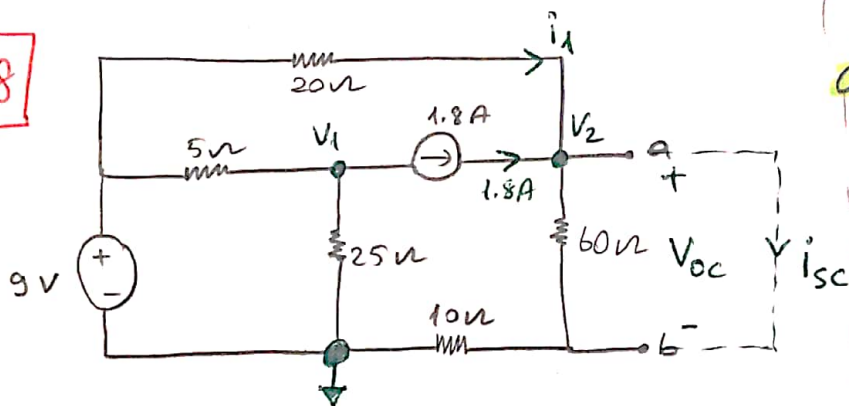

a)

V_{oc}


$$\frac{V_2 - 9}{20} + \frac{V_2}{70} - 1.8 = 0$$

$$V_2 = 35V$$

$$V_{Th} = \frac{60}{60 + 10} \cdot 35 = \underline{\underline{30V}}$$

$$V_{Th} = V_{oc}$$

b)

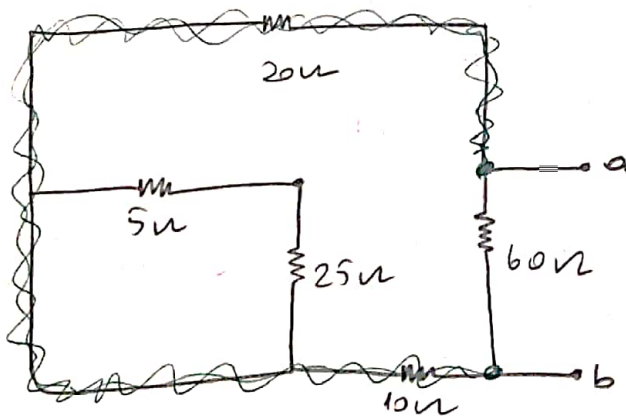

$$R_{Th} = 60 \parallel (20 + 10)$$

$$R_{Th} = \frac{60 \cdot 30}{60 + 30} = \frac{60 \cdot 30}{90} = \underline{\underline{20\Omega}}$$

i_{sc}

$$\frac{V_2 - 9}{20} + \frac{V_2}{10} - 1.8 = 0$$

$$V_2 = 15V$$


$$i_1 = \frac{9 - 15}{20} = -0.3A$$

$$i_{sc} = (1.8 + i_1) = \underline{\underline{1.5A}}$$

$$R_{Th} = \frac{30}{1.5} = 20\Omega$$

4.82

10

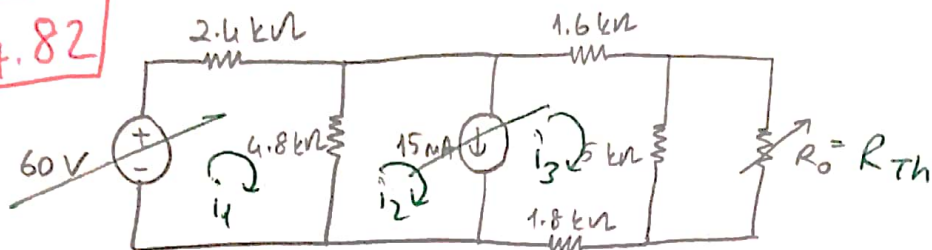

a) Find $R_{Th} \Rightarrow [(2.4k \parallel 4.8k) + 1.6k + 1.8k] \parallel 5k \rightarrow R_{Th} = 2.5k\Omega$

b) $7.2k i_1 - 4.8k i_2 = 60$

$-4.8k i_1 + 4.8k i_2 + 8.4i_3 = 0$


$i_2 - i_3 = 15mA$

$i_1 = 19.4mA$

$i_2 = 16.6mA$

$i_3 = 1.6mA$

$V_{Th} = 5k i_3 = 8V$

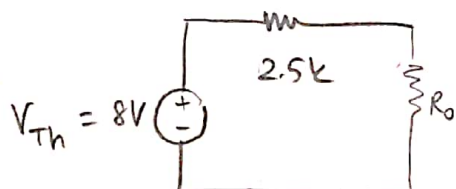


$P_{R_o} = I^2 R = (0.0016)^2 \cdot 2500$
 $= 0.0064 \text{ watt}$

c) Closest to $2.5k$ is $\rightarrow 2.7k\Omega$


$V_{2.7k} = \frac{2.7k}{2.7k + 2.5k} \cdot 8 = 4.15V$

$P_{2.7k} = \frac{V^2}{R} = \frac{(4.15)^2}{2700} = 0.006 \text{ W}$

4.95

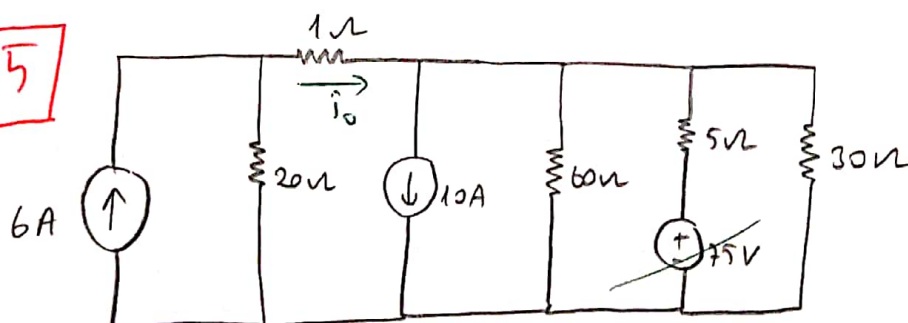


For 6A current source

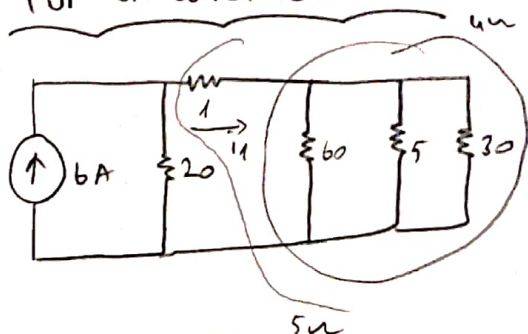

$30 \parallel 5 \parallel 60 = 4\Omega$


$i_1 = \frac{20}{20 + 5} \cdot 6 = 4.8A$

For 10A current source

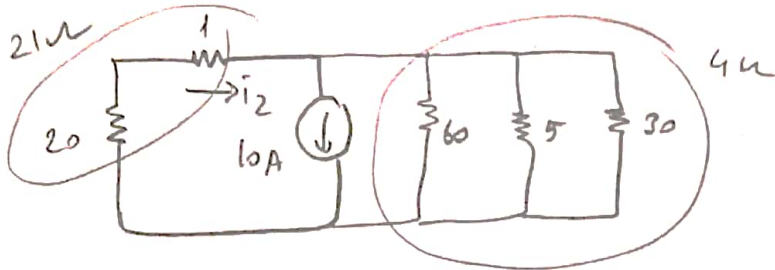

$$i_2 = \frac{4}{21+4} \cdot 10 = 1.6 \text{ A}$$


For 75 voltage source

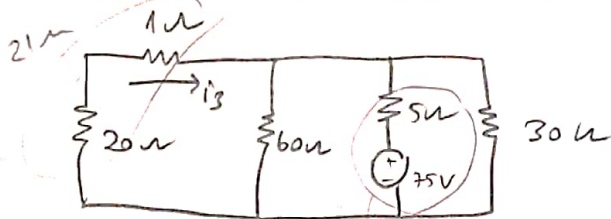

$$V = IR$$

$$75 = I \cdot 5$$

$$I = 15$$

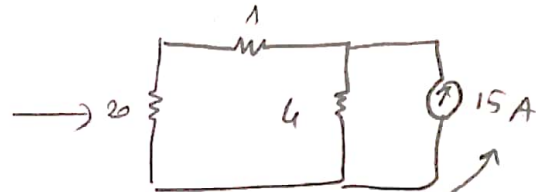

$$i_3 = \frac{4}{25} \cdot 15 = 2.4 \text{ A}$$

Ters yön old. için


$$-2.4 \text{ A}$$

$$i_0 = i_1 + i_2 + i_3 = 4.8 + 1.6 - 2.4$$


$$= 4 \text{ A}$$

EasyEDA simulations


• 4.11

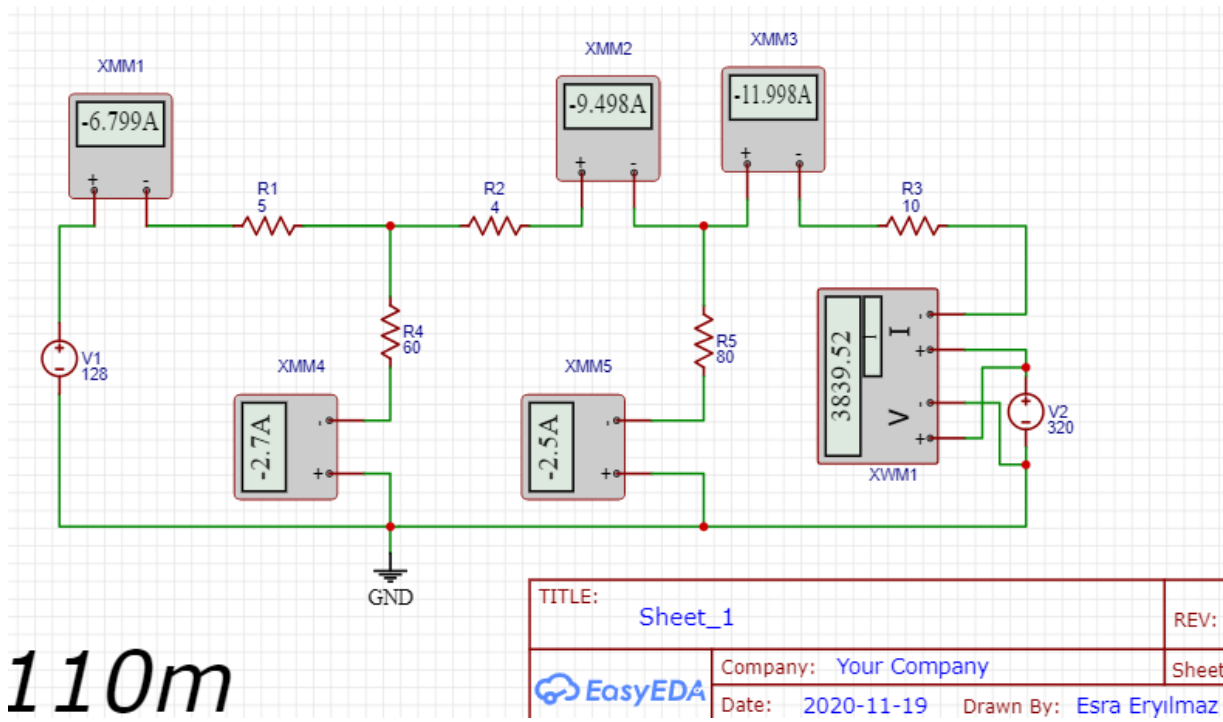


• 4.12

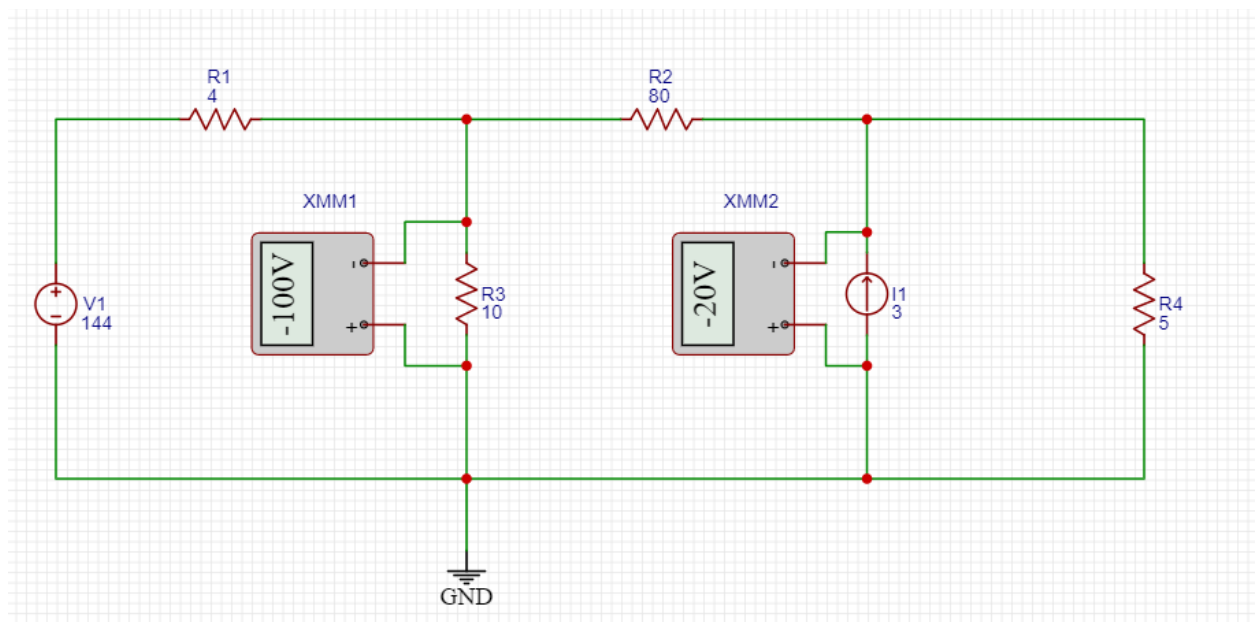


• 4.15

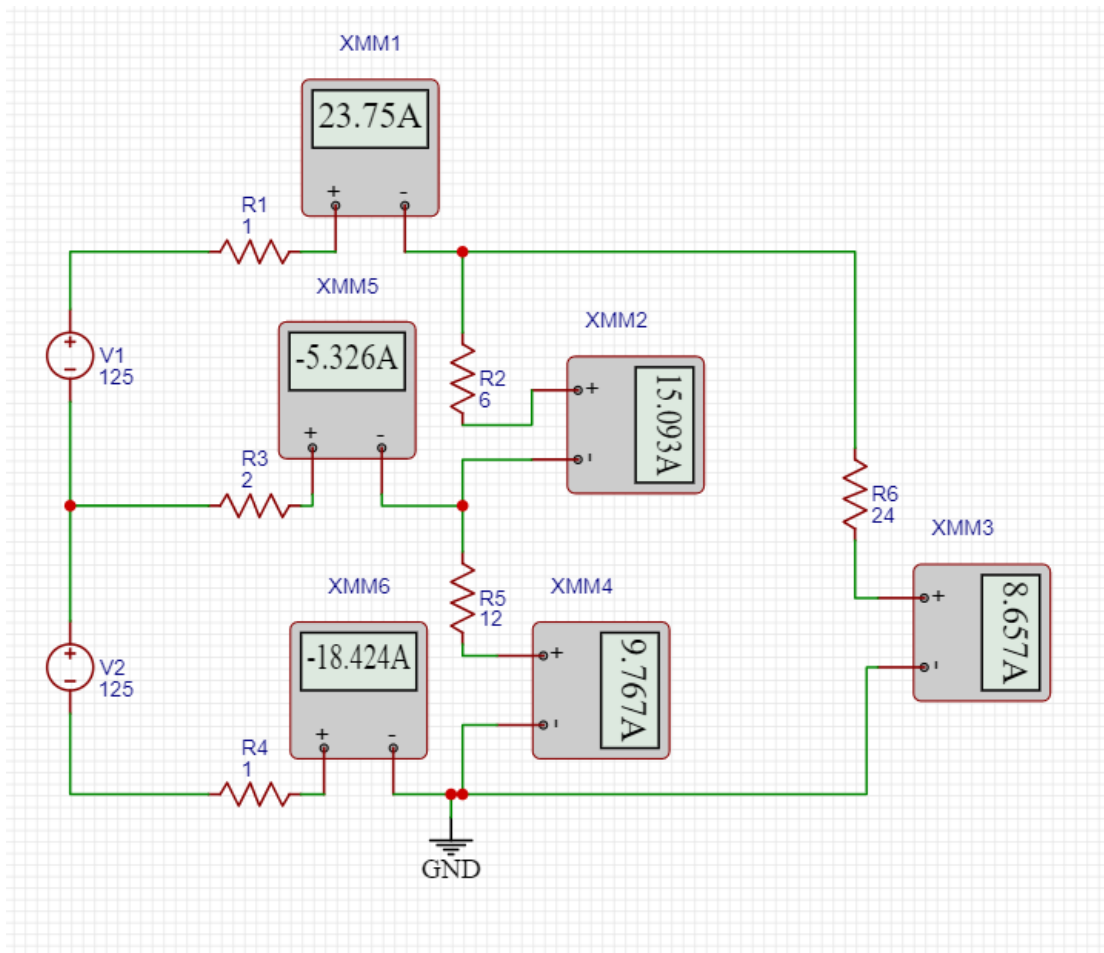


• 4.24

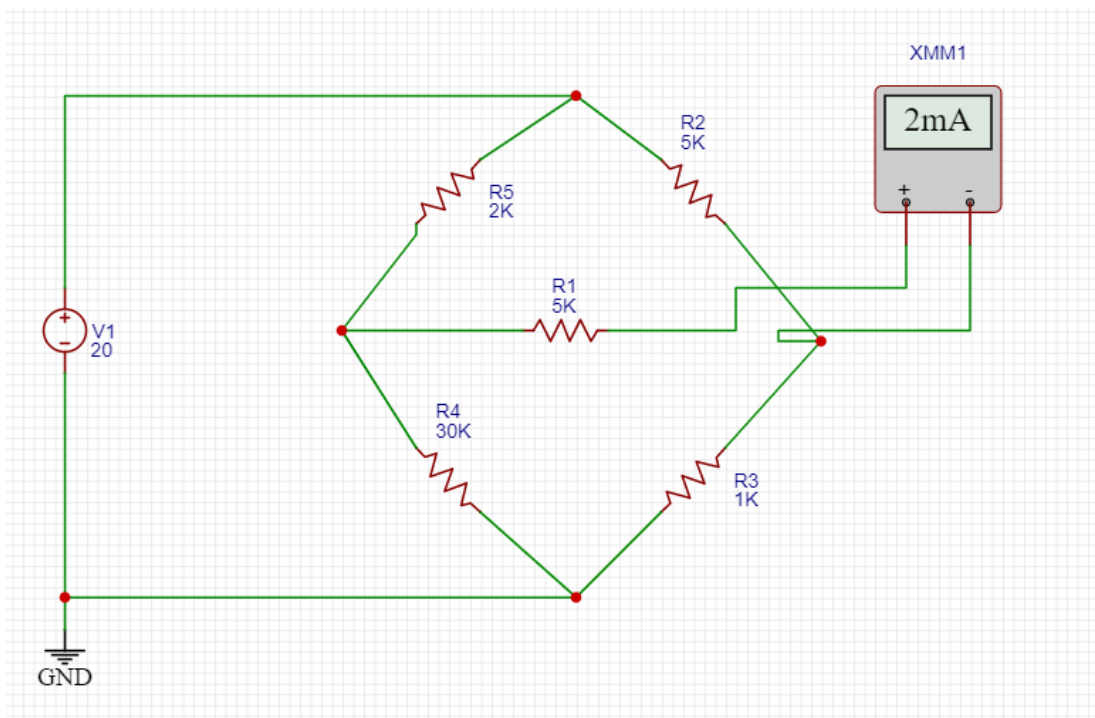


- 4.27

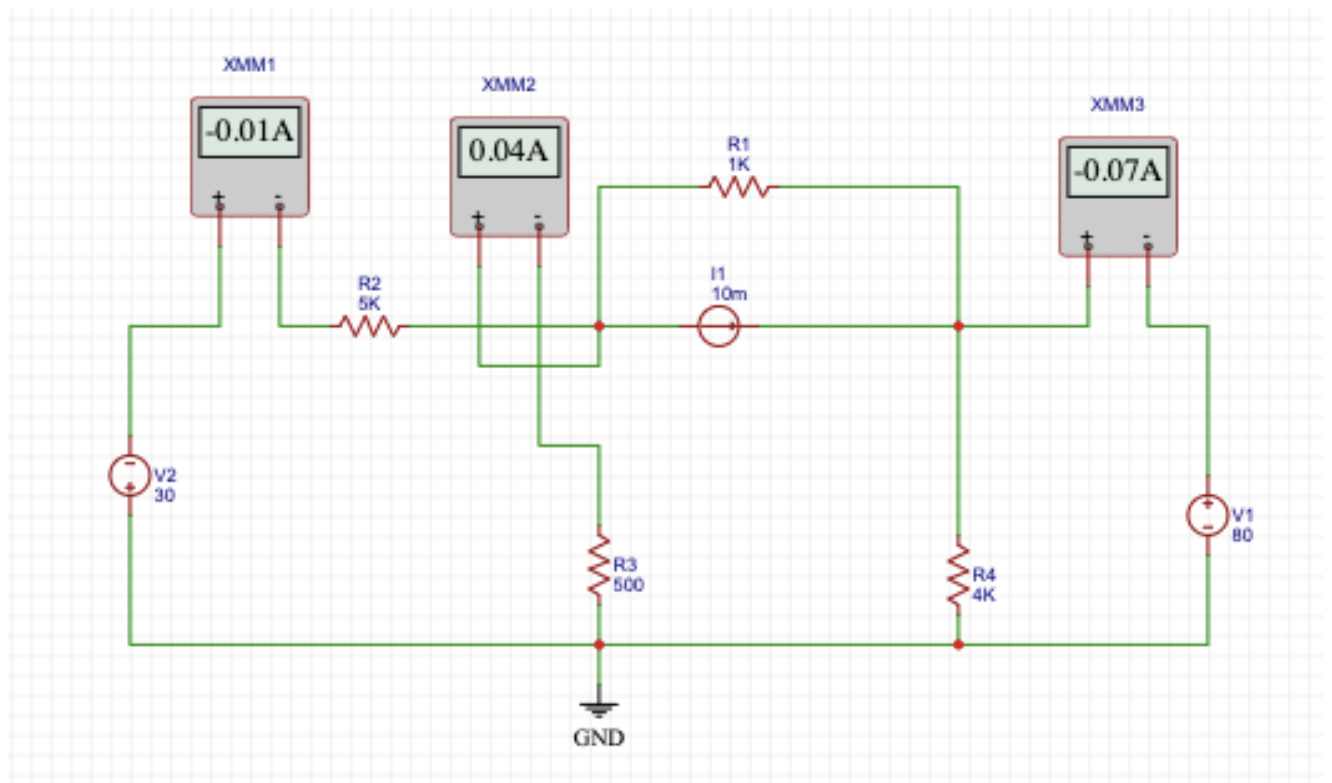


- 4.30

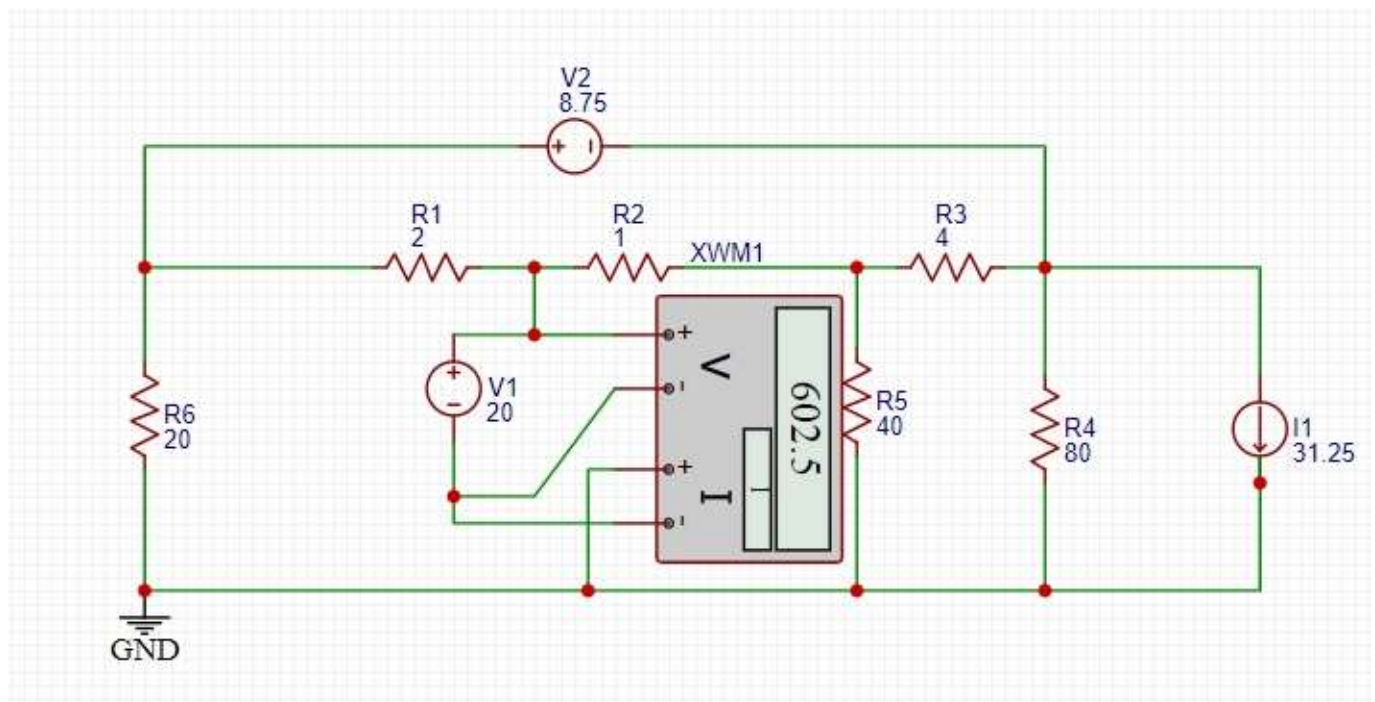


• 4.36

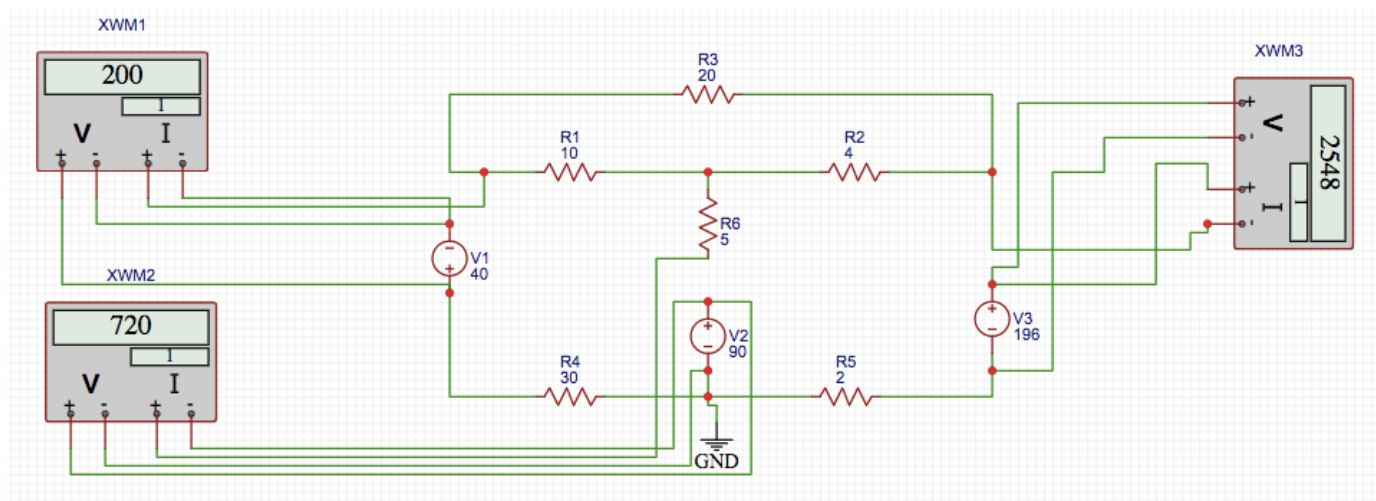


• 4.39

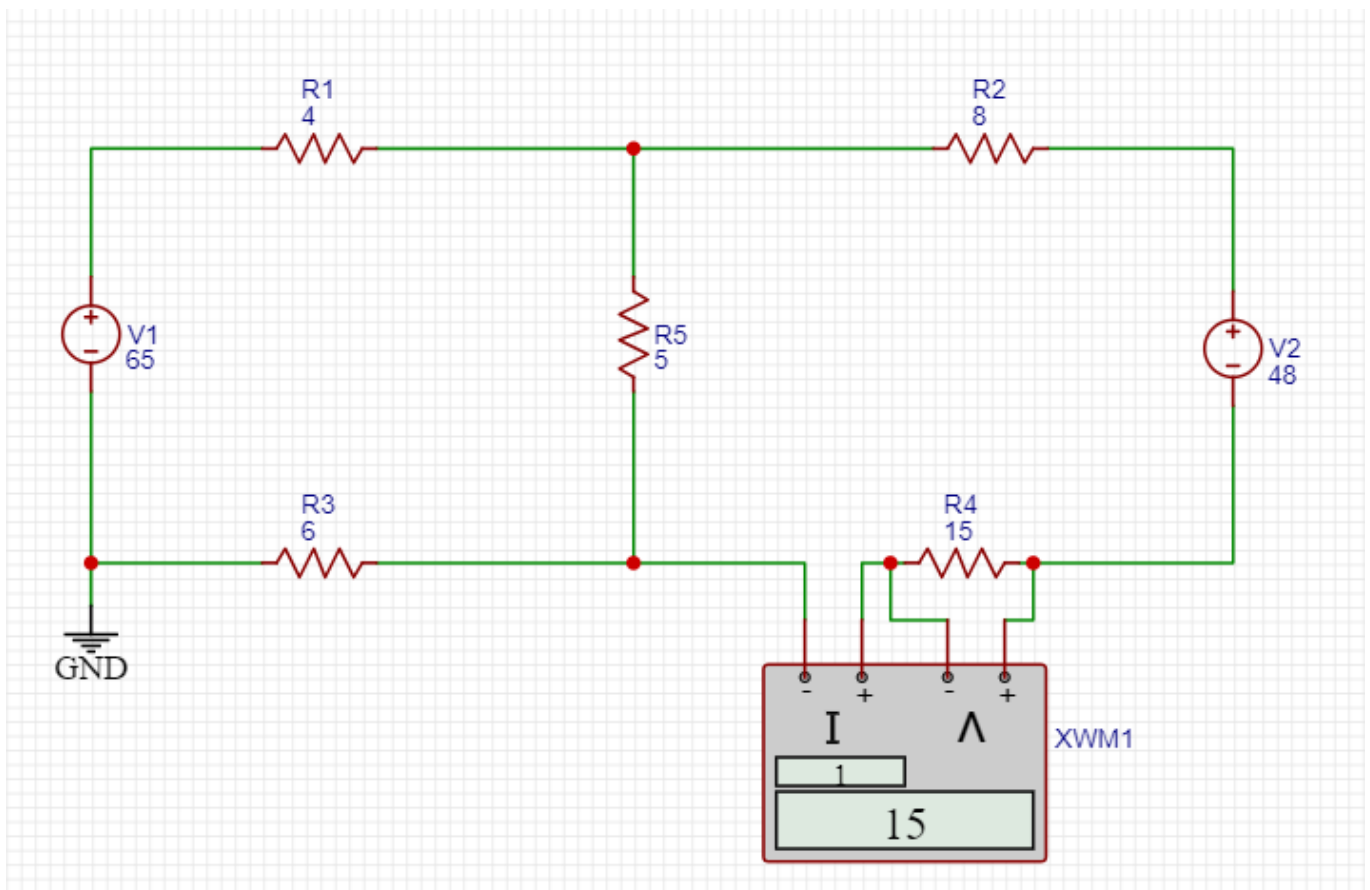


• 4.46

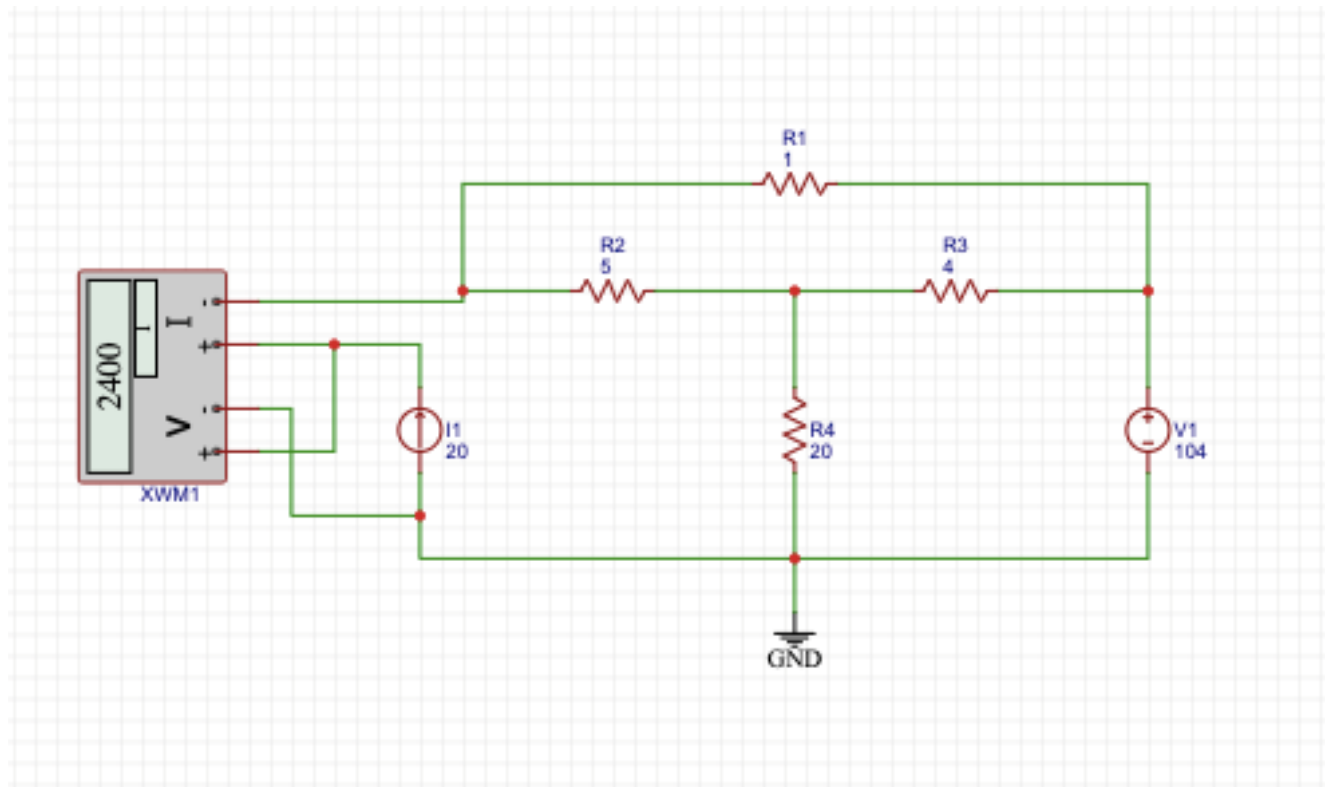


• 4.54

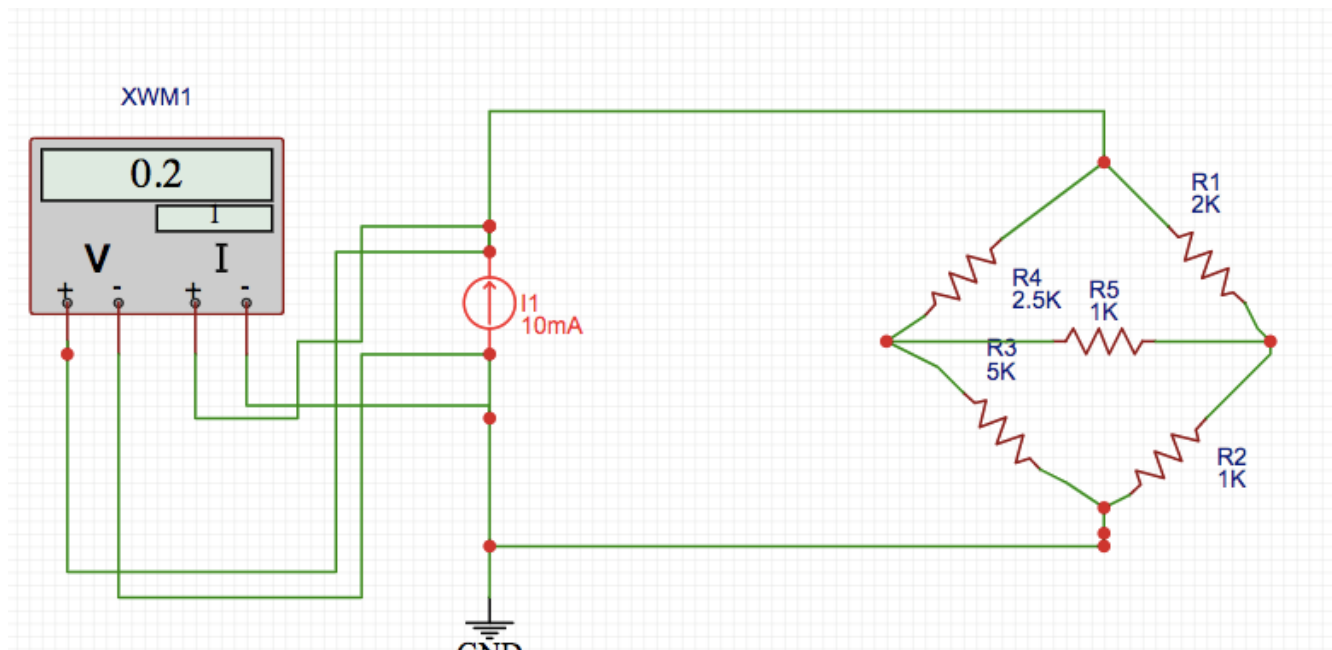


• 4.64

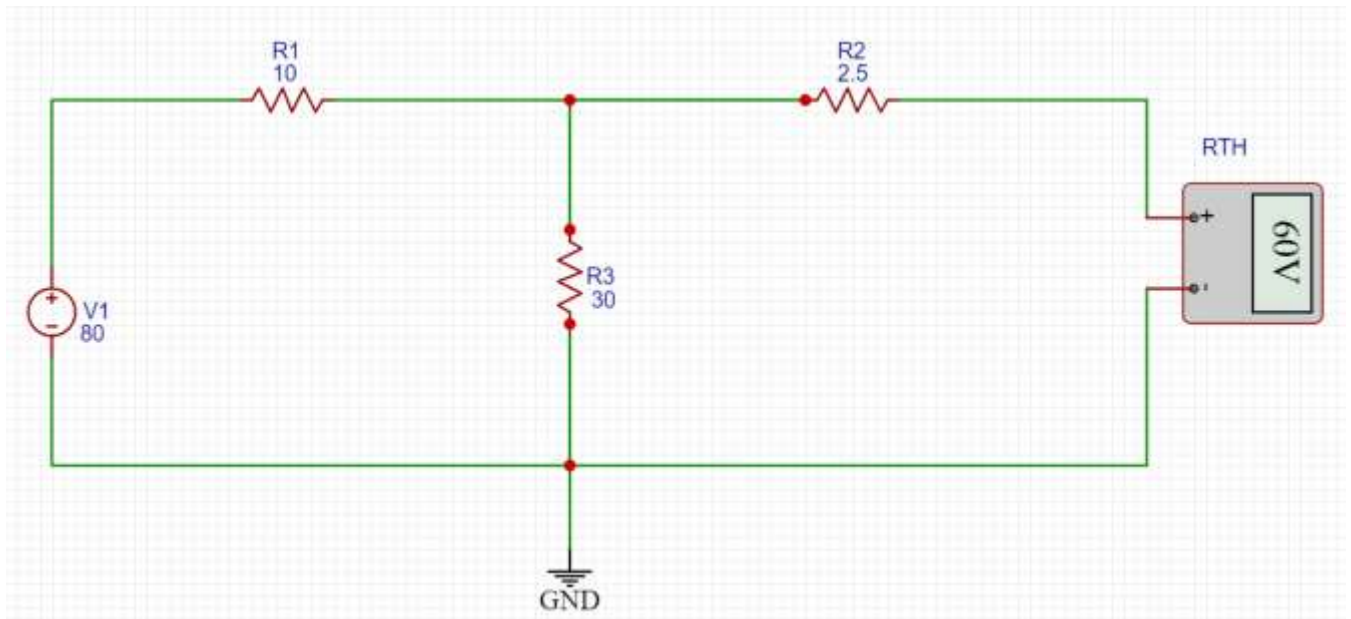

• 4.78

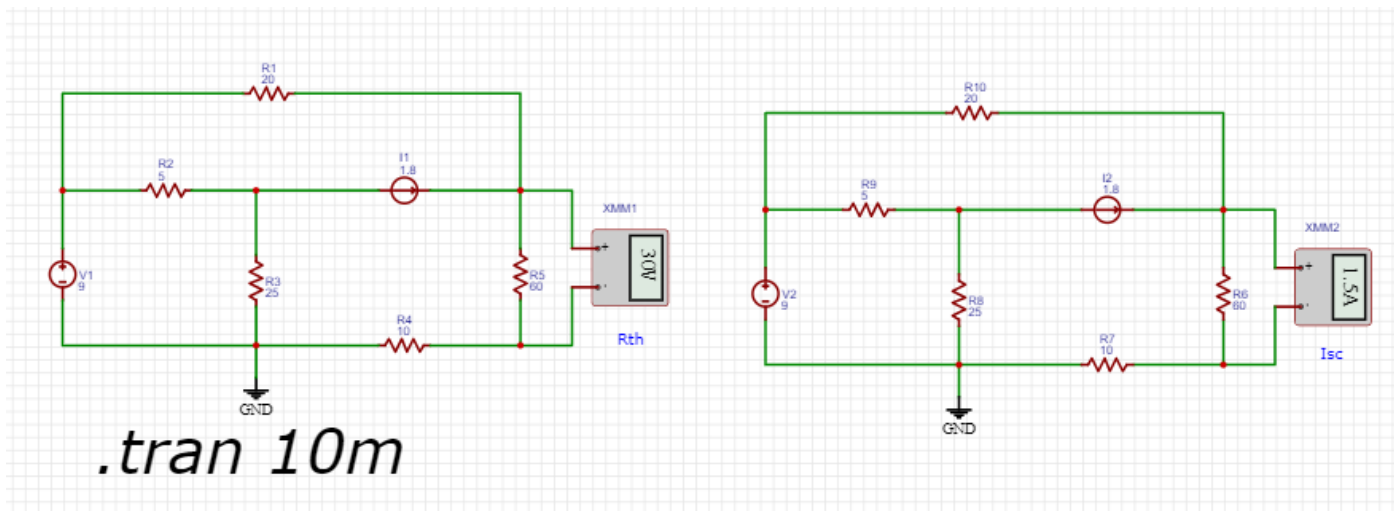

• 4.82

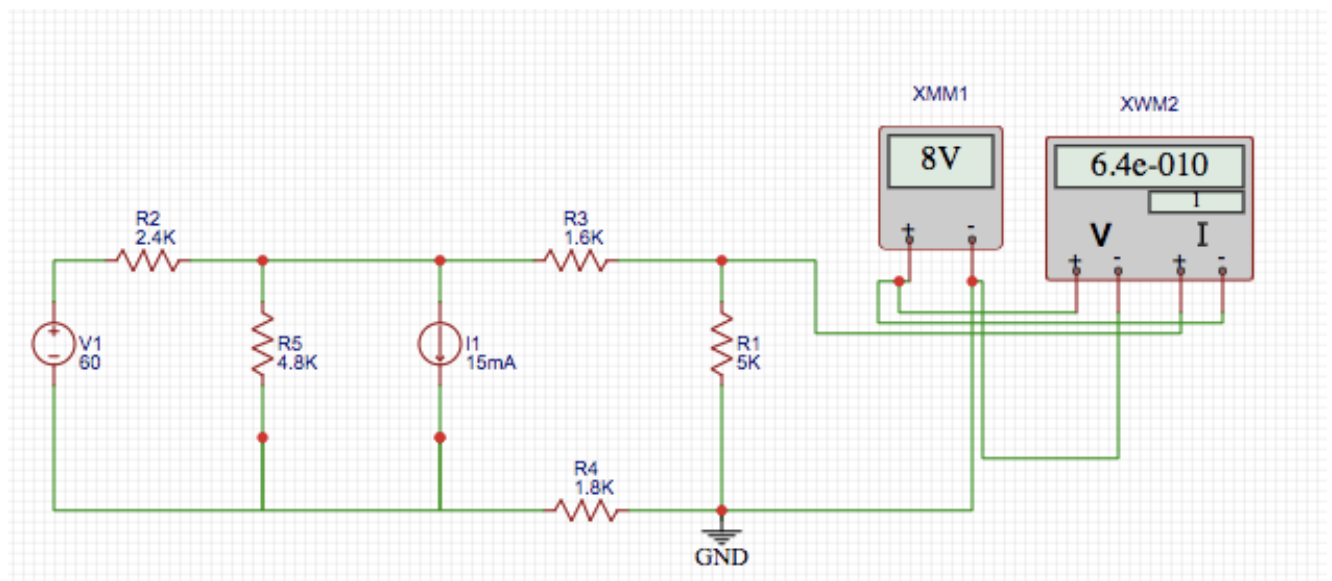

• 4.95

