

CSE231 HW #3

In the book, Nilsson and Riedel "Electric Circuits" 10th ed. (Not the Global Edition), solve the following problems.

- 8.11
- 8.27
- 8.35
- 8.47
- 8.54
- 9.32
- 9.45
- 9.46
- 9.55
- 9.62

Students must solve them on paper, then scan and create a PDF report by using apps like Adobe Scan, Cam Scanner, etc.

Deadline: 31/12/2020 - 23:55

Corresponding Teaching Assistants:

umit.akkaya@gtu.edu.tr

sametgul@gtu.edu.tr