CSE231 HW #2

In the book, Nilsson, Riedel *"Electric Circuits"* 10th ed. (Not the Global Edition) solve the following problems and simulate the ones having (PSPICE|MULTISIM) label using EasyEDA simulation software.

- 4.1
- 4.2
- 4.3
- 4.4
- 4.11
- 4.12
- 4.15
- 4.24
- 4.27
- 4.30

- 4.36
- 4.39
- 4.46
- 4.47
- 4.54
- 4.59
- 4.64
- 4.78
- 4.82
- 4.95

Students should solve them on paper, then scan and create a PDF report using apps like Adobe Scan, Cam Scanner, etc., and add simulation results to the PDF report.

Deadline 20/11/2020 11:55AM (Noon)

Corresponding Teaching Assistants:

- umit.akkaya@gtu.edu.tr
- m.kilinc@gtu.edu.tr
- sametgul@gtu.edu.tr